

$$u = U\sqrt{2} \sin(\omega t + \alpha)$$

$$i = I\sqrt{2} \sin(\omega t + \beta)$$

$$\alpha - \beta = \varphi$$

$$\underline{Z} = \frac{\underline{U}}{\underline{I}} = \frac{U \cdot e^{j\alpha}}{I e^{j\beta}} = \frac{U}{I} e^{j(\alpha - \beta)} = \frac{U}{I} e^{j\varphi}$$

$$\underline{Z} = \underbrace{\left( \frac{U}{I} \cos \varphi \right)}_R + j \underbrace{\left( \frac{U}{I} \sin \varphi \right)}_X$$

$$\underline{Z} = R + jX$$

$$\underline{Y} = \frac{1}{\underline{Z}} = \frac{1}{R + jX} \quad \text{admitanță}$$

$$\underline{Y} = G - jB$$

$\downarrow$  conductanță  
 $\downarrow$  susceptanță

Relații între parametrii unui dipol <sup>pt EXAMEN</sup>

$$\hookrightarrow \underline{Y} = \frac{R - jX}{R^2 + X^2} \quad \left\{ \begin{array}{l} G = \frac{R}{R^2 + X^2} \\ B = \frac{X}{R^2 + X^2} \end{array} \right.$$

$$\underline{Z} = \frac{1}{\underline{Y}} = \frac{G + jB}{G - jB} = \frac{G + jB}{G^2 + B^2} \quad \left\{ \begin{array}{l} R = \frac{G}{G^2 + B^2} \\ X = \frac{B}{G^2 + B^2} \end{array} \right.$$

$$\underline{Z} \underline{Y} = 1$$

$$(R + jX)(G - jB) = 1$$

$$RG + BX = 1$$

$$XG - RB = 0 \Rightarrow \frac{X}{R} = \frac{B}{G}$$

$$\frac{R}{X} = \frac{G}{B}$$